


ANURAG GROUP OF INSTITUTIONS**(Autonomous)****School of Engineering****II-B.Tech-I-Semester End Examinations, October / November - 2019****Subject: Electrical Circuit Analysis****(Only for EEE)****Time: 3 Hours****Max.Marks:75****Section – A (Short Answer type questions)****(25 Marks)**

- Answer All questions
- 1. Give some applications of Milliman's theorem. 2M
- 2. State and explain reciprocity theorem. 3M
- 3. Define incidence and reduced incidence matrix. 2M
- 4. Distinguish between balanced and unbalanced loads. 3M
- 5. Write inductor and capacitor behavior during steady state condition with initial storage. 3M
- 6. Write the relation between line voltage, phase voltage and line current, phase current in a 3-phase balanced star connected system . 2M
- 7. What is the use of pole-zero diagrams? 2M
- 8. Explain the physical interpretation of complex frequency. 3M
- 9. In a two-port network, $A=6$, $B=2$, $C=4$, $D=2$. Determine h_{11} and h_{22} parameters 2M
- 10. Express reciprocity conditions for h-parameters and Y- parameters. 3M


Section – B(Essay Type questions)**(5x10=50 Marks)**

- Answer all questions, each question carry equal marks.


11. A) Obtain the Thevenin's and Norton's equivalent of the given circuit. 10M

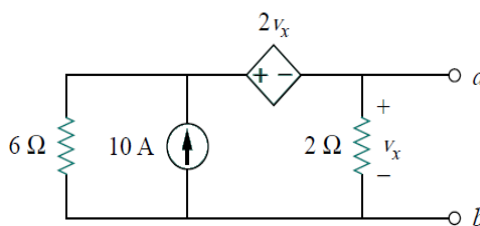**OR**

- B) Using superposition theorem find V_x .

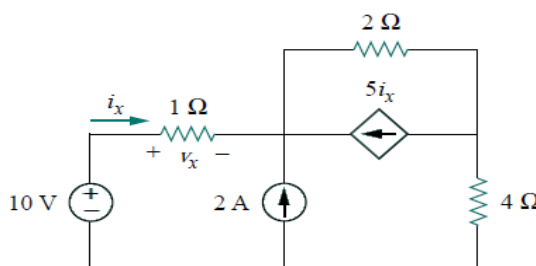
10M

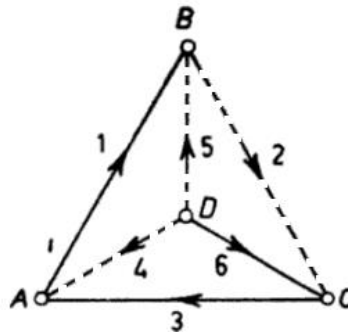12. A) Construct the Basic incidence, basic tie-set and basic cut-set matrices of the following graph. 10M




OR

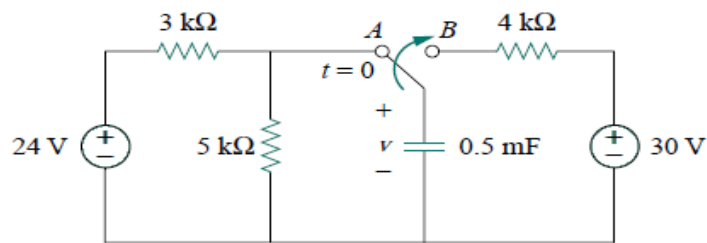- B) Derive the relation between line and phase currents and voltages in a balanced delta connected 3-phase system with neat phasor diagram. 10M
13. A) Derive the transient response of series RC circuit with DC excitation using Differential Approach and Laplace transform approach. 10M
- OR
- B) Determine $v(t)$ at $t > 0$ and calculate its value at $t = 1s$ and $4s$. The switch has been in position A for a long time. At $t = 0$, the switch moves to B. 10M



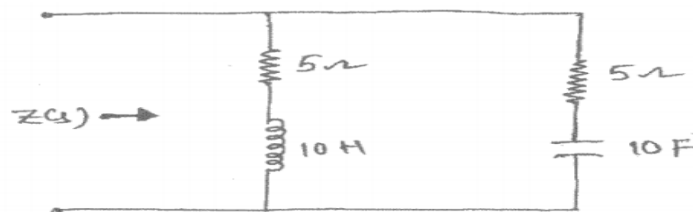14. A) What are poles and zeros of network functions? Obtain pole-zero configuration of the following network. 10M



OR

- B) Mention the necessary conditions for driving point and transfer functions. 10M
15. A) Derive the expression of two port networks connected in parallel and in cascade connection with examples. 10M
- OR
- B) Determine the Z, h-parameters of the network given below. 10M

